

Solutions to the given Assignment Questions :

1 . Ans :

8-bit Register

Verilog Code

```

1
2 //-----Register-----
3
4 `timescale 1ns / 1ps
5 module Multi_register(dout,shift_out,din,ld,clk,shift_in,a_shift,shift_l,shift_r,clr);
6
7 parameter N = 8;
8
9 input [N-1:0] din;
10 input ld,clk,shift_in,shift_l,shift_r,a_shift,clr;
11 output reg shift_out;
12 output reg [N-1:0] dout;
13
14 always @(posedge clk)
15 begin
16
17 if(clr == 1'b1) dout <= 8'b0;
```

```

18
19 else if(ld) dout <= din;
20
21 else if(a_shift == 1'b1)
22 begin
23 dout <= {dout[N-1],dout[N-1:1]};
24 shift_out <= dout[0];
25 end
26
27 else if(shift_l == 1'b1)
28 begin
29 dout <= {dout[N-2:0],shift_in};
30 shift_out <= dout[N-1];
31 end
32
33 else if(shift_r == 1'b1)
34 begin
35 dout <= {shift_in,dout[N-1:1]};
36 shift_out <= dout[0];
37 end
38
39 else dout <= dout;
40
41 end
42
43 endmodule
44
45 //-----TestBench-----
46
47 `timescale 1ns / 1ps
48 module tst;
49
50 // Inputs
51 reg [7:0] din;
52 reg ld;
53 reg clk;
54 reg shift_in;
55 reg a_shift;
56 reg shift_l;
57 reg shift_r;
58 reg clr;
59
60 // Outputs
61 wire [7:0] dout;
62 wire shift_out;
63
64 // Instantiate the Unit Under Test (UUT)
65 Multi_register uut (
66 .dout(dout),
67 .shift_out(shift_out),
68 .din(din),
69 .ld(ld),
70 .clk(clk),
71 .shift_in(shift_in),
72 .a_shift(a_shift),
73 .shift_l(shift_l),
74 .shift_r(shift_r),
75 .clr(clr)
76 );


```

```

77
78 initial begin
79
80 clk= 0;
81 forever #50 clk = ~clk;
82
83 end
84
85 initial begin
86 // Initialize Inputs
87 din = 0;
88 ld = 0;
89 shift_in = 0;
90 a_shift = 1'bz;
91 shift_l = 1'bz;
92 shift_r = 0;
93 clr = 0;
94
95 // Wait 100 ns for global reset to finish
96 //Q,s_out_Q,m_in_2,ldQ,clk,s_out_A,NC,NC,shiftQ,clrQ
97 //dout,shift_out,din,ld,clk,shift_in,a_shift,shift_l,shift_r,clr
98 #100;
99 #10
100 din = 8'b10101011;
101 #100
102 clr = 1'b0;
103 #100
104 ld = 1'b1;
105 #100
106 ld = 1'b0;
107 #100
108 shift_r = 1'b1;
109 #100
110 shift_r = 1'b0;
111
112 // Add stimulus here
113
114 end
115
116 endmodule

```

Simulation Results

 


Example of Usage

Please note that this register can be used in multiplication and division using various algorithms. Here we demonstrate multiplication *Booth's Algorithm*.

8 bit Multiplication using *Booth's Algorithm*

The design of 8 bit Booth Multiplier using Datapath and Control Design is presented as follows:

State Diagram

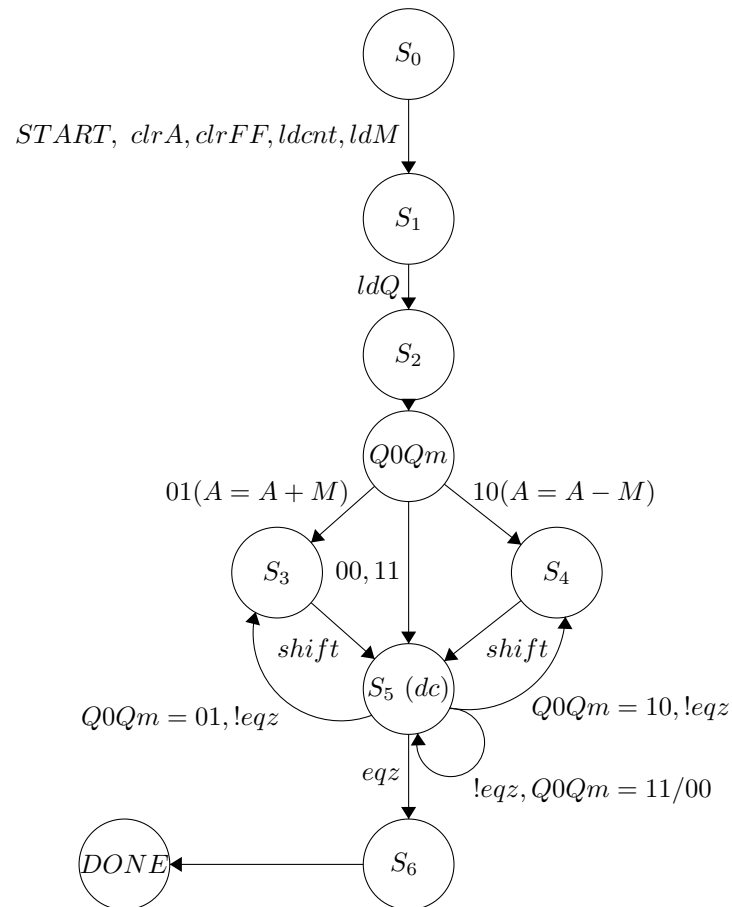

Verilog Code

```
1 //-----COUNTER-----
2
3 `timescale 1ns / 1ps
4 module Counter(out,ldcnt,clk,decr);
5
6 input ldcnt,clk,decr;
7 output reg [3:0] out;
8
9 always @(posedge clk)
10 begin
11
12 if(ldcnt == 1'b1) out <= 4'b1001;
```

```

13 else if(decr == 1'b1) out <= out-1;
14
15 end
16
17 endmodule
18
19
20
21 //-----ALU-----
22
23 `timescale 1ns / 1ps
24 module ALU(out,in1,in2,addsub);
25
26 parameter N =8;
27 input [N-1:0] in1,in2;
28 input addsub;
29
30 output reg [N-1:0] out;
31
32 always @(*)
33 begin
34
35 if(addsub == 1'b0) out <= in1 - in2;
36 else out <= in1 + in2;
37
38 end
39
40
41 endmodule
42 //-----REGISTER-----
43
44 `timescale 1ns / 1ps
45 module Multi_register(dout,shift_out,din,ld,clk,shift_in,a_shift,shift_l,shift_r,clr);
46
47 parameter N = 8;
48
49 input [N-1:0] din;
50 input ld,clk,shift_in,shift_l,shift_r,a_shift,clr;
51 output reg shift_out;
52 output reg [N-1:0] dout;
53
54 always @(posedge clk)
55 begin
56
57 if(clr == 1'b1) dout <= 8'b0;
58
59 else if(ld) dout <= din;
60
61 else if(a_shift == 1'b1)
62 begin
63 dout <= {dout[N-1],dout[N-1:1]};
64 shift_out <= dout[0];
65 end
66
67 else if(shift_l == 1'b1)
68 begin
69 dout <= {dout[N-2:0],shift_in};
70 shift_out <= dout[N-1];
71 end

```

```

72
73 else if(shift_r == 1'b1)
74 begin
75 dout <= {shift_in,dout[N-1:1]};
76 shift_out <= dout[0];
77 end
78
79 else dout <= dout;
80
81 end
82
83 endmodule
84 //-----D FLIPFLOP-----
85
86 `timescale 1ns / 1ps
87 module D_FF(Q,D,clk,clr);
88
89 input D,clk,clr;
90 output reg Q;
91
92 always @(posedge clk)
93 begin
94
95 if(clr == 1'b1) Q <= 1'b0;
96
97 else Q <= D;
98
99 end
100
101 endmodule
102
103 //-----DATAPATH-----
104
105 `timescale 1ns / 1ps
106 module mul_datapath(out_A,out_Q,Qm,eqz,Q0,ldA,ldQ,clrA,shiftA,
107 clrQ,shiftQ,ldM,clrFF,addsub,clk,m_in_1,m_in_2,ldcnt,decr);
108
109 output Qm,Q0,eqz;
110 parameter N = 8;
111 parameter NC = 1'bz;
112 output [N-1:0] out_A,out_Q;
113 input [N-1:0] m_in_1,m_in_2;
114 input ldA,ldQ,ldM,clrA,clrQ,clrFF,shiftA,shiftQ,clk,addsub,ldcnt,decr;
115 wire [N-1:0] A,M,Q,Z;
116 wire [3:0] count;
117 wire s_out_A,s_out_Q,dum;
118
119 assign Q0 = Q[0];
120 assign eqz = ~|count;
121 assign out_A = A;
122 assign out_Q = Q;
123
124 Multi_register A1(A,s_out_A,Z,ldA,clk,NC,shiftA,NC,NC,clrA);
125 Multi_register Q1(Q,s_out_Q,m_in_2,ldQ,clk,s_out_A,NC,NC,shiftQ,clrQ);
126
127 D_FF RQ(Qm,s_out_Q,clk,clrFF);
128
129 Multi_register M1(M,dum,m_in_1,ldM,clk,NC,NC,NC,NC,NC);
130

```

```

131 ALU Alu1(Z,A,M,addsub);
132
133 Counter C1(count,ldcnt,clk,decr);
134
135 endmodule
136
137
138
139
140
141 //-----CONTROLPATH-----
142
143 `timescale 1ns / 1ps
144 module mul_controlpath(ldA,ldQ,DONE,
145 ldcnt,decr,ldM,clrA,clrQ,clrFF,addsub,shiftA,shiftQ,Q0,Qm,eqz,clk,START);
146
147 input Q0,Qm,clk,eqz,START;
148 output reg ldA,ldQ,ldcnt,ldM,decr,addsub,DONE,clrA,clrQ,clrFF,shiftA,shiftQ;
149
150 reg [2:0] state;
151
152 parameter S0 = 3'b000,S1 = 3'b001, S2 = 3'b010, S3 = 3'b011, S4 = 3'b100, S5 = 3'b101,S6 = 3'b110;
153
154 always @(posedge clk)
155
156 begin
157
158 case(state)
159
160
161 S0 : if(START) state <= S1;
162 S1 : state <= S2;
163 S2 : begin
164 case({Q0,Qm})
165
166 2'b10 : state <= S4;
167 2'b01 : state <= S3;
168 default : state <= S5;
169 endcase
170
171 end
172 S3 : state <= S5;
173 S4 : state <= S5;
174 S5 : begin
175 if(({Q0,Qm} == 2'b10) && !eqz) state <= S4;
176 else if(({Q0,Qm} == 2'b01) && !eqz) state <= S3;
177 else if(({Q0,Qm} == 2'b11)||({Q0,Qm} == 2'b00)) && !eqz) state <= S5;
178 else if(eqz) state <= S6;
179 end
180
181 S6 : state <= S6;
182
183 default : state <= S0;
184
185 endcase
186
187 end
188
189 always @(state)

```

```

190
191 begin
192
193 case(state)
194
195 S0 : begin
196   clrA = 1'b0;
197   clrQ = 1'b0;
198   clrFF = 1'b0;
199   ldA = 1'b0;
200   ldQ = 1'b0;
201   ldM = 1'b0;
202   decr = 1'b0;
203   shiftA = 1'b0;
204   shiftQ = 1'b0;
205 end
206
207 S1 : begin
208   clrA = 1'b1;
209   clrFF = 1'b1;
210   ldM = 1'b1;
211   ldcnt = 1'b1;
212 end
213
214 S2 : begin
215   clrA = 1'b0;
216   clrFF = 1'b0;
217   ldM = 1'b0;
218   ldcnt = 1'b0;
219   ldQ = 1'b1;
220 end
221
222 S3 : begin
223   addsub = 1'b1;
224   ldA = 1'b1;
225   ldQ = 1'b0;
226   shiftA = 1'b0;
227   shiftQ = 1'b0;
228   decr = 1'b0;
229 end
230
231 S4 : begin
232   addsub = 1'b0;
233   ldA = 1'b1;
234   ldQ = 1'b0;
235   shiftA = 1'b0;
236   shiftQ = 1'b0;
237   decr = 1'b0;
238 end
239
240 S5 : begin
241   ldA = 1'b0;
242   ldQ = 1'b0;
243   shiftA = 1'b1;
244   shiftQ = 1'b1;
245   decr = 1'b1;
246 end
247
248 S6 :      begin

```



```

249 DONE  = 1'b1;
250 decr= 1'b0;
251 shiftA= 1'b0;
252 shiftQ= 1'b0;
253 ldA= 1'b0;
254 end
255
256
257 default : begin
258 clrA = 1'b0;
259 shiftA = 1'b0;
260 ldQ = 1'b0;
261 shiftQ = 1'b0;
262 end
263 endcase
264
265 end
266
267
268 endmodule
269 //-----MAIN MODULE-----
270
271 `timescale 1ns / 1ps
272 module Booth_Multiplier(out,START,M1,M2,clk);
273
274 parameter N = 8;
275 output reg [2*N-1:0] out;
276 input [N-1:0] M1,M2;
277 input clk,START;
278
279
280 wire ldA,ldQ,ldM,shiftA,shiftQ,ldcnt,decr,clrA,clrQ,clrFF,addsub,DONE,Q0,QM,eqz;
281 wire [N-1:0] out1,out2;
282
283 mul_controlpath CON(ldA,ldQ,DONE,ldcnt,decr,ldM,clrA,clrQ,
284 clrFF,addsub,shiftA,shiftQ,Q0,Qm,eqz,clk,START);
285 mul_datapath DAT(out1,out2,Qm,eqz,Q0,ldA,ldQ,clrA,
286 shiftA,clrQ,shiftQ,ldM,clrFF,addsub,clk,M1,M2,ldcnt,decr);
287
288 always @(posedge clk)
289 begin
290
291 if(DONE == 1'b1) out <= {out1,out2};
292
293 end
294
295 endmodule
296 //-----TEST BENCH-----
297
298 `timescale 1ns / 1ps
299 module TEST;
300
301 // Inputs
302 reg START;
303 reg [7:0] M1;
304 reg [7:0] M2;
305 reg clk;
306
307 // Outputs


```

```



308 wire [15:0] out;
309
310 // Instantiate the Unit Under Test (UUT)
311 Booth_Multiplier uut (
312     .out(out),
313     .START(START),
314     .M1(M1),
315     .M2(M2),
316     .clk(clk)
317 );
318
319 initial begin
320     clk = 0;
321     forever #50 clk = ~clk;
322
323 end
324
325 initial begin
326     // Initialize Inputs
327     START = 0;
328     M1 = 0;
329     M2 = 0;
330
331
332     // Wait 100 ns for global reset to finish
333     #100;
334     #10
335
336     M1 = 8'b000000101;
337     M2 = 8'b000000100;
338
339     #10
340
341     START = 1'b1;
342
343     #100
344     START = 1'b0;
345
346
347     // Add stimulus here
348
349 end
350
351 endmodule

```

Simulation Results :

 

Schematic :

  

Please note the register can be similarly used for Multiplication and Division using various other algorithms.