

Figure 1: Zoomed Schematic

2 . Ans :

Verilog Code using Structural Style :

```

1  //-----STRUCTURAL STYLE-----
2
3
4  /// ALU
5  -----
6  `timescale 1ns / 1ps
7  module ALU(A,B,CO,S1,S0,M,C_out,data_out
8  );
9  parameter N = 4;
10 parameter ZERO = 4'b0000;
11 input  [N-1:0] A,B;
12 input  S1,S0,M,CO;
13 output [N-1:0] data_out;
14 output C_out;
15
16 wire [N-1:0] AND,OR,XOR,XNOR,PASS,SUM,DIFF1,DIFF2;
17 wire cand,cor,cxor,cxnor,cpass,csum,cdiff1,cdiff2;

```

```

18 wire [N-1:0] comp_A, comp_B;
19
20 andop M0(A,B,AND);
21 assign cand = 1'bz;
22 orop M1(A,B,OR);
23 assign cor = 1'bz;
24 xorop M2(A,B,XOR);
25 assign cxor = 1'bz;
26 xnorop M3(A,B,XNOR);
27 assign cxnor = 1'bz;
28 ripple_adder A0(A,ZERO,C0,cpass,PASS);
29 ripple_adder A1(A,B,C0,csum,SUM);
30 compop CB(B,comp_B);
31 ripple_adder A3(A,comp_B,C0,cdiff1,DIFF1);
32 compop CA(A,comp_A);
33 ripple_adder A4(comp_A,B,C0,cdiff2,DIFF2);
34
35 mux8to1 M81({cand,AND},{cor,OR},{cxor,XOR},{cxnor,XNOR},{cpass,PASS},{csum,SUM},{cdiff1,DIFF1},{cdiff2,DIFF2});
36
37 endmodule
38
39 // AND MODULE
40 -----
41 `timescale 1ns / 1ps
42 module andop(A,B,C
43 );
44 parameter N=4;
45 input [N-1:0] A,B;
46 output [N-1:0] C;
47 genvar p;
48
49 generate
50 for(p = 0; p<N; p = p+1)
51 begin : and1p
52 and AG(C[p],A[p],B[p]);
53 end
54 endgenerate
55
56 endmodule
57 // OR MODULE
58 -----
59 `timescale 1ns / 1ps
60 module orop(A,B,C
61 );
62 parameter N=4;
63 input [N-1:0] A,B;
64 output [N-1:0] C;
65 genvar p;
66
67 generate
68 for(p = 0; p<N; p = p+1)
69 begin : or1p
70 or OG(C[p],A[p],B[p]);
71 end
72 endgenerate
73
74
75 endmodule
76 // XOR MODULE

```

```

77 -----
78 `timescale 1ns / 1ps
79 module xorop(A,B,C
80 );
81 parameter N=4;
82 input [N-1:0] A,B;
83 output [N-1:0] C;
84 genvar p;
85
86 generate
87 for(p = 0; p<N; p = p+1)
88 begin : xor1p
89 xor XG(C[p],A[p],B[p]);
90 end
91 endgenerate
92
93
94 endmodule
95 //XNOR MODULE
96 -----
97 `timescale 1ns / 1ps
98 module xnorop(A,B,C
99 );
100 parameter N=4;
101 input [N-1:0] A,B;
102 output [N-1:0] C;
103 genvar p;
104
105 generate
106 for(p = 0; p<N; p = p+1)
107 begin : xn1p
108 xnor XNG(C[p],A[p],B[p]);
109 end
110 endgenerate
111
112
113 endmodule
114
115 //COMPLEMENT MODULE
116 -----
117 `timescale 1ns / 1ps
118 module compop(A,C
119 );
120 parameter N=4;
121 input [N-1:0] A;
122 output [N-1:0] C;
123 genvar p;
124
125 generate
126 for(p = 0; p<N; p = p+1)
127 begin : complp
128 not NG(C[p],A[p]);
129 end
130 endgenerate
131
132
133 endmodule
134
135 // FULL ADDER

```

```

136 -----
137 `timescale 1ns / 1ps
138 module full_adder(A,B,Cin,Cout,S
139 );
140 input A,B,Cin;
141 output Cout,S;
142
143 wire [2:0] w;
144
145 xor X1(w[0],A,B), X2(S,w[0],Cin);
146 and A1(w[1],A,B), A2(w[2],w[0],Cin);
147 or R1(Cout,w[1],w[2]);
148
149 endmodule
150
151 // RIPPLE ADDER
152 -----
153 `timescale 1ns / 1ps
154 module ripple_adder(A,B,Cin,Cout,S
155 );
156 parameter N = 4;
157 input [N-1:0] A,B;
158 input Cin;
159 output [N-1:0] S;
160 output Cout;
161 wire [N:0] carry;
162 assign carry[0] = Cin;
163 assign Cout = carry[N];
164
165 genvar p;
166 generate
167 for(p=0;p<N;p=p+1)
168 begin : fa_loop
169 full_adder FA(A[p],B[p],carry[p],carry[p+1],S[p]);
170 end
171 endgenerate
172
173
174 endmodule
175
176 // MUX 2X1
177 -----
178 `timescale 1ns / 1ps
179 module mux2to1(in0,in1,sel,out
180 );
181 parameter N = 5;
182 input [N-1:0] in1,in0;
183 input sel;
184 output [N-1:0] out;
185
186 assign out = (sel == 1'b0)? in0 : in1;
187
188
189 endmodule
190
191 //MUX 4X1
192 -----
193 `timescale 1ns / 1ps
194 module mux4to1(in0,in1,in2,in3,sel,out

```

```

195 );
196 parameter N = 5;
197 input [N-1:0] in3,in2,in1,in0;
198 input [1:0] sel;
199 output [N-1:0] out;
200 wire [N-1:0] t1,t0;
201
202 mux2to1 M0(in0,in1,sel[0],t0);
203 mux2to1 M1(in2,in3,sel[0],t1);
204 mux2to1 M2(t0,t1,sel[1],out);
205
206 endmodule
207
208 // MUX 8X1
209 -----
210 `timescale 1ns / 1ps
211 module mux8to1(in0,in1,in2,in3,in4,in5,in6,in7,sel2,sel1,sel0,out
212 );
213
214 parameter N = 5;
215 input [N-1:0] in0,in1,in2,in3,in4,in5,in6,in7;
216 input sel2,sel1,sel0;
217 output [N-1:0] out;
218 wire [N-1:0] t1,t0;
219
220 mux4to1 M0(in0,in1,in2,in3,{sel1,sel0},t0);
221 mux4to1 M1(in4,in5,in6,in7,{sel1,sel0},t1);
222 mux2to1 M2(t0,t1,sel2,out);
223
224 endmodule
225
226 // -----TEST BENCH-----
227 `timescale 1ns / 1ps
228 module TEST;
229
230 // Inputs
231 reg [3:0] A;
232 reg [3:0] B;
233 reg C0;
234 reg S1;
235 reg S0;
236 reg M;
237
238 // Outputs
239 wire C_out;
240 wire [3:0] data_out;
241
242 // Instantiate the Unit Under Test (UUT)
243 ALU uut (
244 .A(A),
245 .B(B),
246 .C0(C0),
247 .S1(S1),
248 .S0(S0),
249 .M(M),
250 .C_out(C_out),
251 .data_out(data_out)
252 );
253


```

```


254  initial begin
255  // Initialize Inputs
256  A = 0;
257  B = 0;
258  C0 = 0;
259  S1 = 0;
260  S0 = 0;
261  M = 0;
262
263  // Wait 100 ns for global reset to finish
264  #100;
265  A = 4'b1100;
266  B = 4'b1010;
267  C0 = 0;
268  S1 = 0;
269  S0 = 0;
270  M = 0;
271  #100
272  A = 4'b1100;
273  B = 4'b1100;
274  C0 = 0;
275  S1 = 0;
276  S0 = 1;
277  M = 1;
278  #100;
279  A = 4'b1100;
280  B = 4'b1010;
281  C0 = 0;
282  S1 = 1;
283  S0 = 0;
284  M = 0;
285  #100
286  A = 4'b1001;
287  B = 4'b1000;
288  C0 = 1;
289  S1 = 1;
290  S0 = 0;
291  M = 1;
292  #100
293  A = 4'b0100;
294  B = 4'b0110;
295  C0 = 1;
296  S1 = 1;
297  S0 = 1;
298  M = 1;
299  #100
300  A = 4'b0100;
301  B = 4'b0110;
302  C0 = 1;
303  S1 = 1;
304  S0 = 0;
305  M = 1;
306
307  // Add stimulus here
308
309  end
310
311  endmodule

```

Simulation Results :

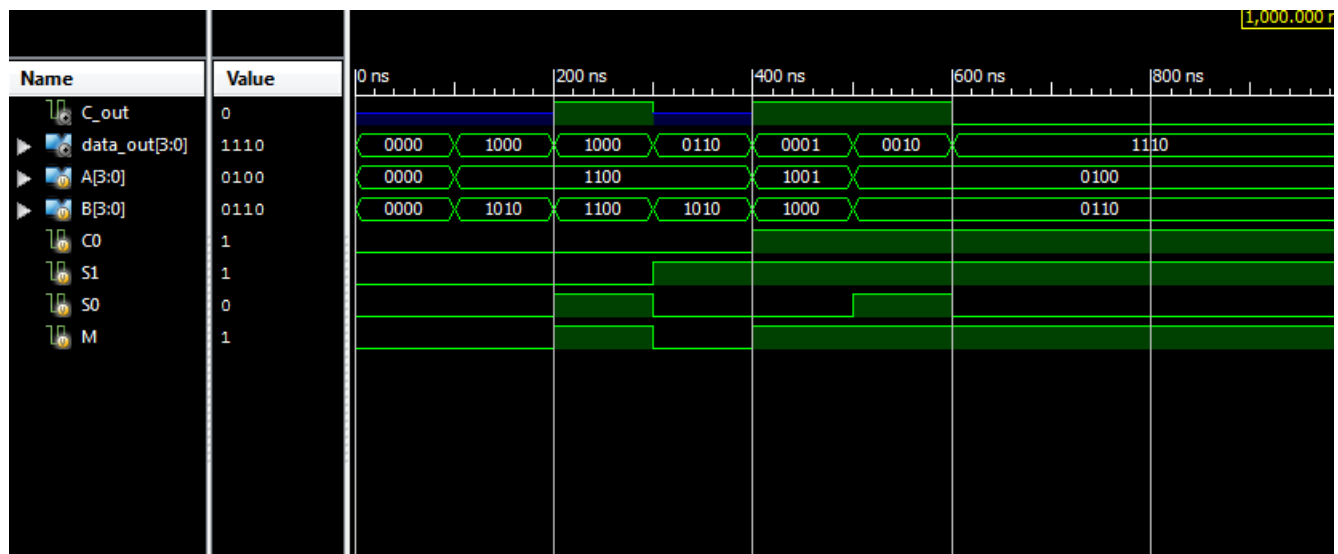

Schematic :

 

 


Figure 2: Block Level Schematic

 


Figure 3: Fully Blown out Schematic

Remarks

- Please note that the output can be followed by the bcd to 7 segment converter for displaying the output on a 7 segment display.
- The remaining user constraints can be added, for displaying the output as mentioned and it can be implemented on FPGA.

3 . Ans :

Verilog Code using Structural Style :

```
1 //-----
2 //-----Carry Save Adder-----
3 //----- (with ripple carry adder in final stage)-----
4
5
6 //Full adder-----
7 `timescale 1ns / 1ps
8 module full_adder(A,B,Cin,S,Cout
9 );
10 input A,B,Cin;
11 output S,Cout;
12
13 wire [2:0] w;
14
15 xor X1(w[0],A,B),X2(S,Cin,w[0]);
16 and A1(w[1],A,B),A2(w[2],w[0],Cin);
17 or O1(Cout,w[1],w[2]);
18
19 endmodule
20
21
22 //Carry Save Adder-----
23
24 `timescale 1ns / 1ps
25 module carry_save_adder(A,B,S,Cout
26 );
27 parameter N = 8;
28 parameter ZERO = 8'b00000000;
29 input [N-1:0] A,B;
30 output [N-1:0] S;
31 wire [N:0] S2;
32 output Cout;
33
34 wire [N:0] S1,C1;
35 wire [N+1:0] C;
36 assign S = S2[N-1:0];
37 assign C[0] = 1'b0;
```